

II BE Mid Semester Test II 2021
(CS A&B) Engineering
(CER3C4): (DIGITAL ELECTRONICS)

Duration: 70 min

Maximum Marks : 20

Note: Attempt any four questions. All questions are of equal marks.

Q.1) Design BCD to gray code converter for decimal numbers. Determine all the Boolean expressions and draw logic diagram also.

Q.2) Implement a full Subtractor using two half Subtractor and OR gates.

Q.3) Simplify the Boolean function using tabulation method

$$F(A,B,C,D) = \sum (0,1,2,5,8,9,10)$$

Q.4) Explain NAND and NOR implementation using one example for each.

Q.5) What is decoder ? Explain 4x16 decoder with proper logic diagram.